

TI Designs

Gas or Water Meter with Two LC Sensors



TI Designs

TI Designs provide the foundation that you need including methodology, testing and design files to quickly evaluate and customize the system. TI Designs help you accelerate your time to market.

Design Resources

TIDM-LC-WATERMTR	Design Page
MSP430FR6989	Product Folder
MSP430G2333	Product Folder
DRV8837	Product Folder
TPS62237	Product Folder





[ASK Our E2E Experts](#)
[WEBENCH® Calculator Tools](#)

Design Features

- Ultra-Low Power Design
- Contactless Rotation Detection
- Two LC Sensors
- Self-Calibration for Long-Term Operation
- Full Platform Design with Socket for Add-On Module and Flow Emulation by a Motor Board
- Onboard Debugging Circuit

Featured Applications

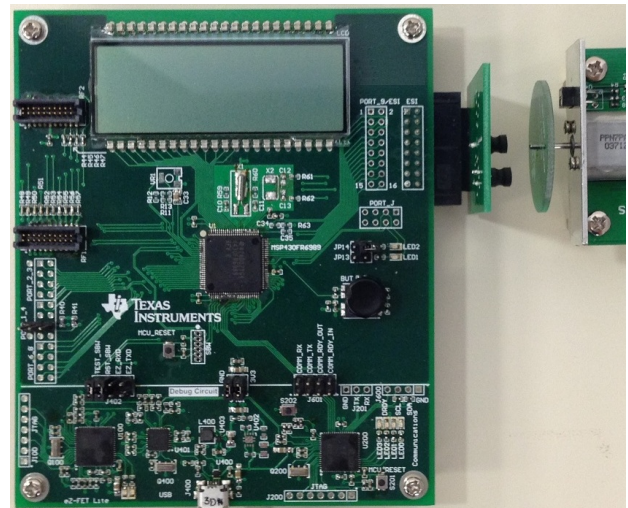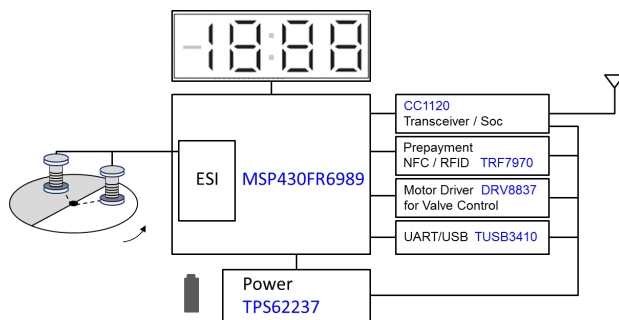- Gas Meter
- Water Meter
- Heat Meter
- Rotation Detection
- Motor Position Detection



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

All trademarks are the property of their respective owners.

1 System Description

This reference design for a rotational flow meter is built using the Extended Scan IF (ESI) of MSP430FR6989, two LC sensors, and the EVM EVM430-FR6989.

The whole EVM can be divided into three boards: the main board, sensor board, and motor board. The main board of the EVM consists of MSP430FR6989, a sensor board connector, an RF module socket, and a debugger circuit. The sensor board is constructed with two LC sensors. The motor board drives a rotor disc to emulate water flow, which moves the rotating disc in a flow meter.

This system is an ultra-low power design using the latest TI MCU MSP430FR6989 with FRAM to store the programming code. The MSP430FR6989 has a built-in module of ESI. The system block diagram shows all the elements that the EVM has and the potential add-on modules, like the RF sub-system or the NFC/RFID module, that can be connected to the EVM ([Figure 2](#)).

The main board of EVM consists of MSP430FR6989, a socket for add-on module, USB connection, and a sensor board connector. The bottom side of the main board features an onboard eZ-FET lite connected to the MCU. Program and debug the MCU firmware by directly connecting the board with a USB cable to PC. The IDE is TI's Code Composer Studio™. The debugging circuit also consists of an HID connection, which can receive the command of a dedicated PC GUI for this EVM.

2 Design Features

2.1 Ultra-Low Power Design

MSP430FR6989 is an ultra-low power MCU that has a FRAM of up to 128 KB for code and data. Peripherals include ESI, RTC, ADC12, CRC, AES256, MPY32, eUSCI for communication, Comp_E for touch key module, an LCD, and six timers.

When operating this design, only the ESI, a timer, and the LCD continuously work with an oscillation crystal of 32,768 Hz. The CPU and other peripherals are off, in low power mode 3 (LPM3). The whole system uses around 7 μ A for a sample rate of 500 Hz with two LC sensors without an LCD.

2.2 Contactless Rotation Detection

When gas or water flows through the meter, the rotating plate inside the meter rotates according to the flow rate. The sensors can detect the number of the plate's rotations without direct contact, which prevents corrosion and safety issues.

2.3 Two-LC Sensor Board

An LC sensor consists of an inductor and a capacitor to form a tank oscillator. This sensor is the proven solution of low power consumption and reliable for the long-term, continuous operation of flow meters. With a very short pulse within 1 μ s, The sensor starts oscillating in its resonant frequency. The inductor then generates a magnetic field. Once the metal part of the rotating plate is cutting the magnetic field, an eddy current is formed in the metal, which will absorb the magnetic energy from the inductor. The amplitude of the oscillating signal will be reduced. The comparator and the DAC of the ESI can detect this change of signal to detect the position of the rotating plate and count the number of rotations.

Two LC sensors are used for the detection of both clockwise and anti-clockwise rotation. A flow meter, like a water meter, has a bounce back of water flow when the tap is closed, making the rotor disc turn backwards and forwards repeatedly before the flow rate becomes zero. To eliminate the counting error of a single sensor, two sensors can count the number of rotations for both directions and give a correct result.

In [Figure 1](#), a logic low is given out when the sensor is detecting the metal part and a logic high when located in the non-metal part. Two sensors are located 90 degrees apart. In this setting, the signal of one sensor will always be 90 degrees out of phase to the other sensor, giving out four states of the two sensors: 00, 01, 11, and 10. The sequence of these four states identify the rotating direction.

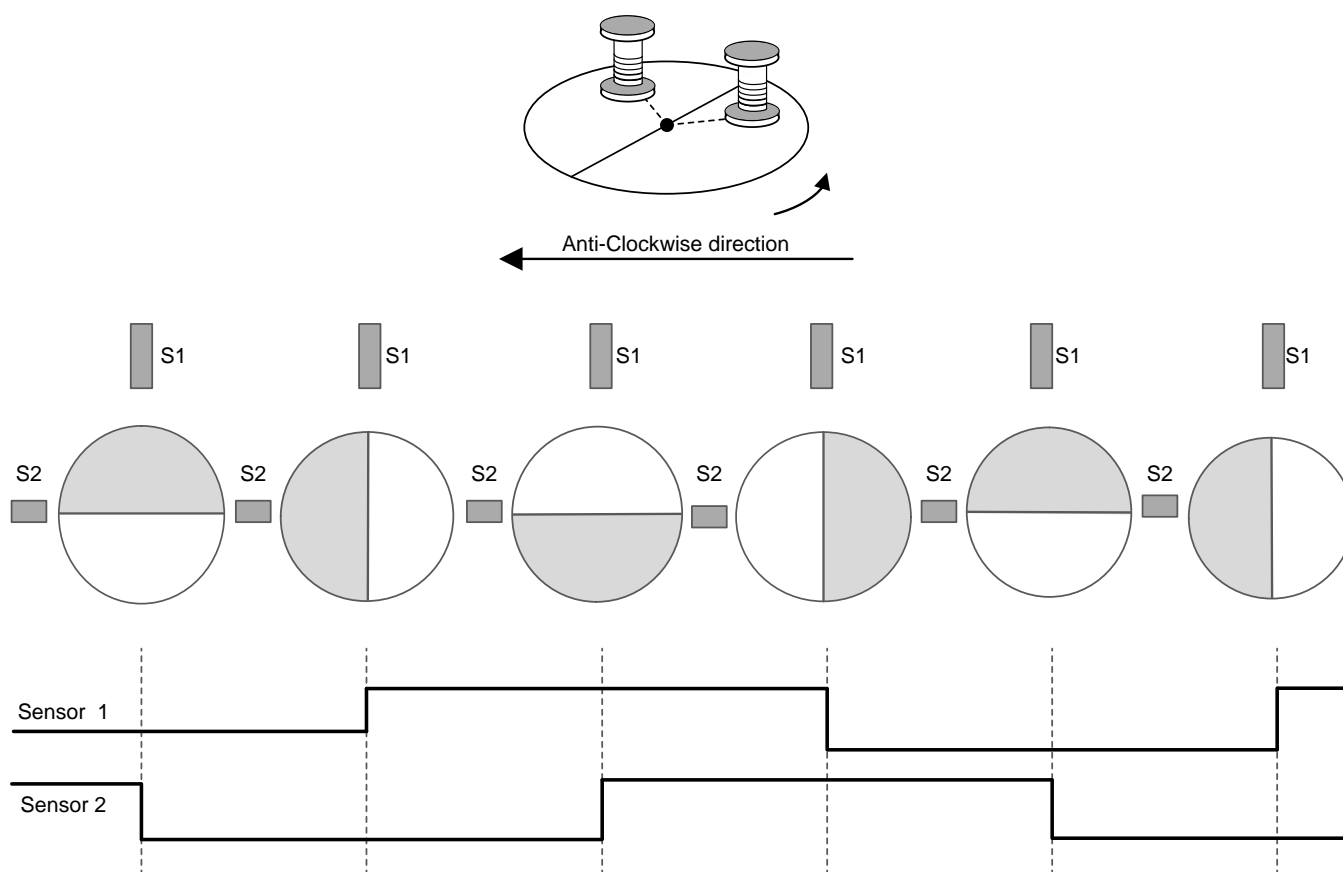


Figure 1. Logic Signal Compiled from LC Sensors

2.4 Self-Calibration for Long-Term Operation

Due to the temperature, humidity, aging components, and signal drifts, a continuous adjustment circuit is necessary to ensure the system is within the range of reliable operation. The ESI has a duplicated circuit inside, which can be used for detecting the overall drift of the system. This circuit will only be activated periodically to save power consumption. Once the drift is found, the circuit adjusts the DAC values of the continuously operating part of the ESI to align it to the signal position of maximum reliability.

2.5 Full Platform Design with Add-On Module Socket and Flow Emulation by a Motor Board

The motor board provides a tool to emulate the rotating plate driven by the flow of gas or water. Adjust the rotating speed either manually or by the main board through the I2C link. The socket connects with various communication ports, SPI, UART, and the I/O of the MCU. Some existing TI RF modules can directly plug into this socket to add on more features to the EVM. Engineers can also design their own modules, like NFC/RFID, valve control, and so on, and test it with the system without reconfiguring the whole board.

The sensor board is standalone. Engineers can design their own customized sensor board and plug into the main board for testing.

2.6 Built-In Debugging Circuit

The built-in debugging circuit facilitates the system setup without too many external connections of debugging tools. The bottom side of the main board has an onboard eZ-FET lite connected to the MCU. Engineers can program and debug the MCU firmware by directly connecting the board with a USB cable to the PC. The IDE is TI's Code Composer Studio™. The debugging circuit also has an HID connection, which can receive the command of a dedicated PC GUI for this EVM.

3 Block Diagram

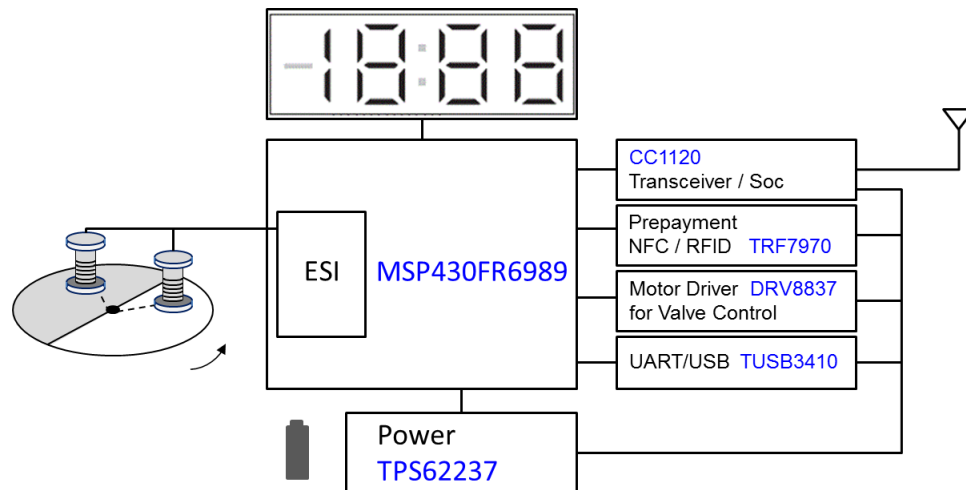


Figure 2. System Block Diagram

4 Circuit Design

4.1 Main Board

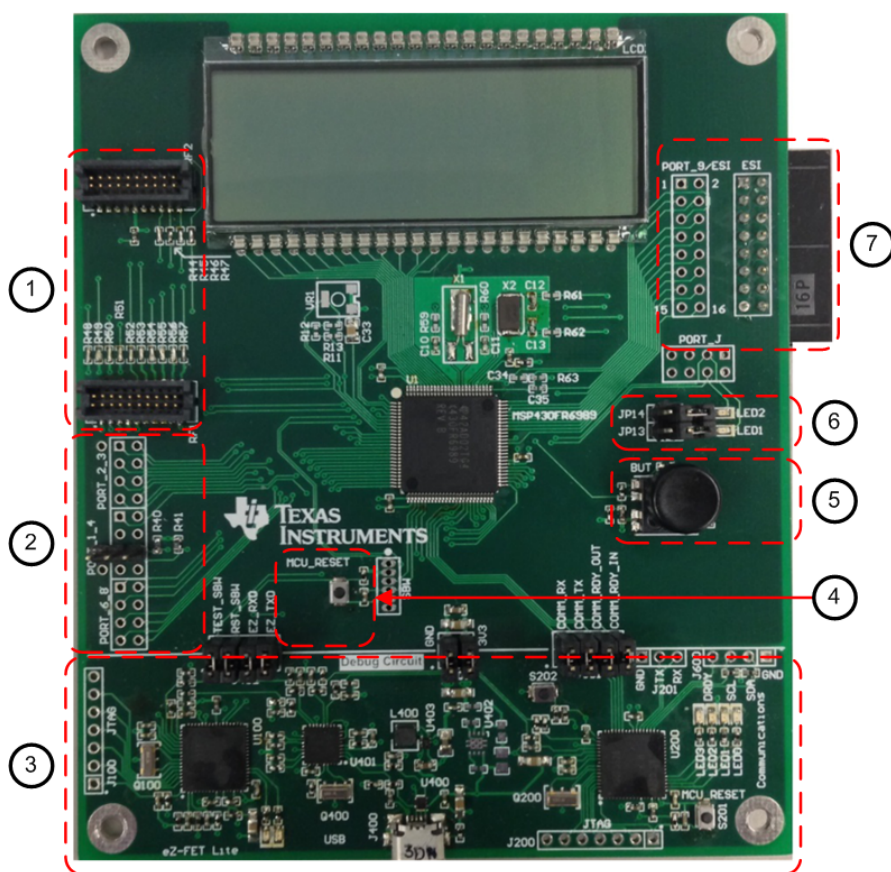


Figure 3. Main Board of EVM

This main board is built on the MCU MSP430FR6989 with an LCD display. This board is powered by USB to provide 3.3 V through a buck converter. This board can be divided into seven parts and is a platform for developing flow meters with RF and USB connections. The application software has code for the ESI module for flow measurement, but the software does not connect to Part 1 and Part 6 in [Table 1](#).

Table 1. Description of Main Board Layout

PART NUMBER	DESCRIPTION
Part 1	A socket for RF modules of sub-1 GHz or 2.4 GHz, connecting to the MCU with SPI and I/O. For details of RF modules, read the CC1120 development kit.
Part 2	Through holes connecting to I/O of no connection. The headers are the I2C connection.
Part 3	The JTAG debugger and a USB HID interface. The HID interface can connect the board to PC with a dedicated GUI.
Part 4	A reset button. This board does not have an on/off switch. To restart the firmware, push the reset button.
Part 5	This device has five push-button switches. The firmware does not have code for this part. Designers can use it to implement a key control.
Part 6	LED indicator, connecting to PJ.2 and PJ.3. For saving current consumption, remove the jumpers.
Part 7	The socket for the sensor board and connecting to the ESI of MCU.

The core part of the hardware for flow measurement is the connection of the MCU's ESI to the sensor board. A 470-nF capacitor connecting to ESICOM stabilizes the voltage of $V_{cc} / 2$. The ESI is a self-contained module inside the MCU.

For a low-power design, a 32,768-Hz crystal is used to continuously operate. To lower the power consumption further, turn on the LCD only when taking a reading is necessary. The rest of the MCU peripherals and its CPU are kept idle to save power. The CPU should only be active during a reading update and self-calibrating, which is done in a periodical manner lasting a few seconds to hours depending on the timer setting.

4.2 Sensor Board

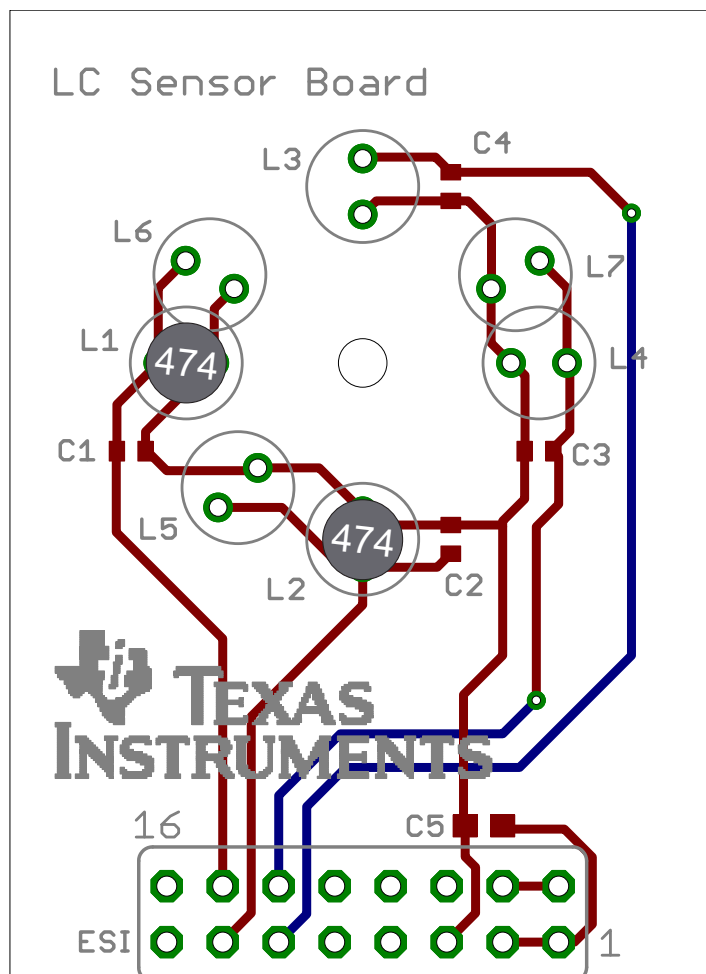


Figure 4. Sensor Board

The sensor board is designed for LC sensors only. The sensors can be placed in different orientations. For the half-covered metal rotor disc, the two sensors are placed 90 degrees apart.

The selection of the inductor (L) and capacitor (C) is an important factor to affect the power consumption. Find a detailed selection guide as an application note for other types of sensors.

4.3 Motor Board

The motor board is to drive the rotor disc to emulate a gas or water flow. The battery socket is on the back of the board. The board consists of the following parts:

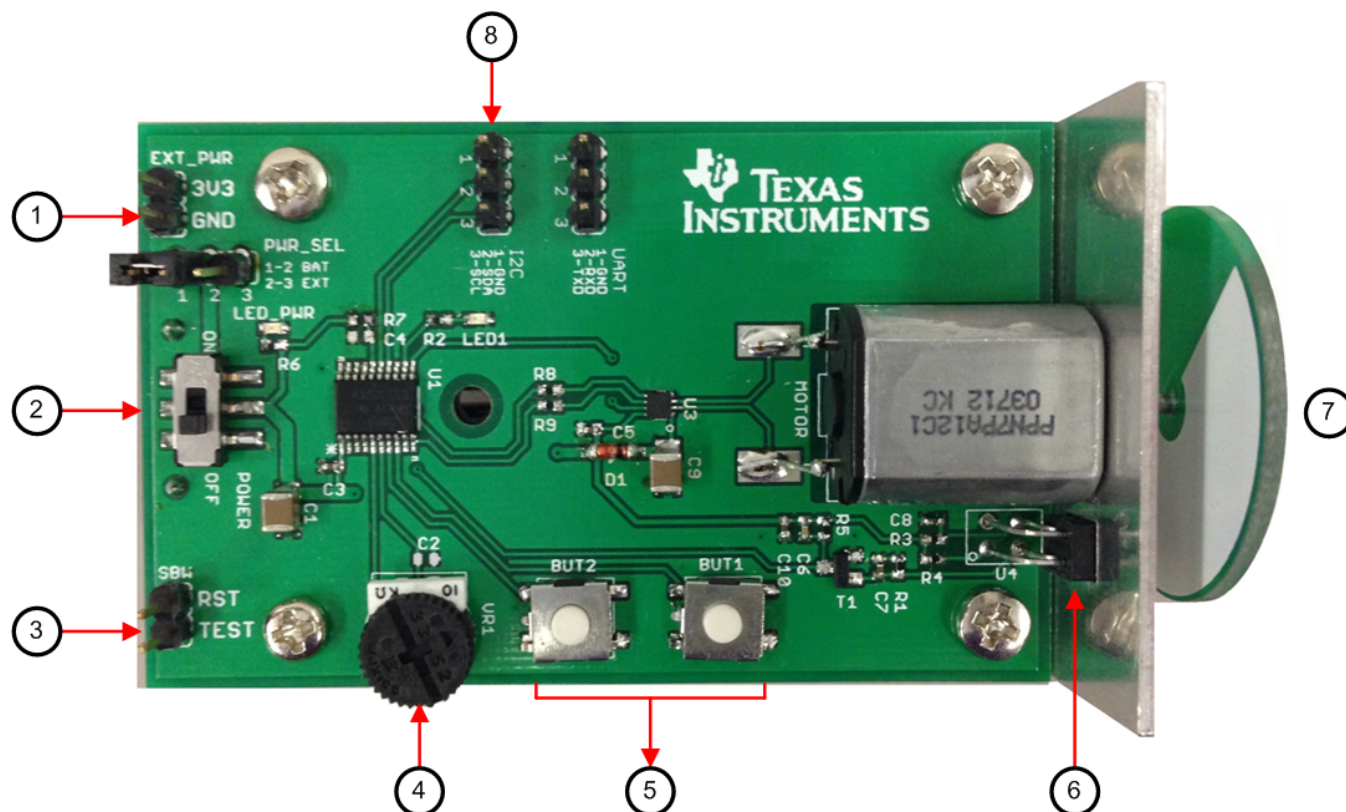


Figure 5. Motor Board

Table 2. Description of Motor Board Layout

PART NUMBER	DESCRIPTION
Part 1	Two pins connecting to external power
Part 2	Switch to power on and off the motor board
Part 3	2-wire (Spy-Bi Wire) mode of JTAG. This mode can be used to program and debug the firmware
Part 4	Variable resistor to vary the rotation speed
Part 5	Buttons to select the rotation's direction. Also acts as a stop button
Part 6	An infrared sensor that provides feedback on the rotation speed of the rotor disc
Part 7	A rotor disc half covered by copper
Part 8	A connection header for I2C and UART

An I2C link can connect to the main board. The motor board will receive the command from main board to rotate in a proper speed and send back the record of the number of rotations.

5 Software Description

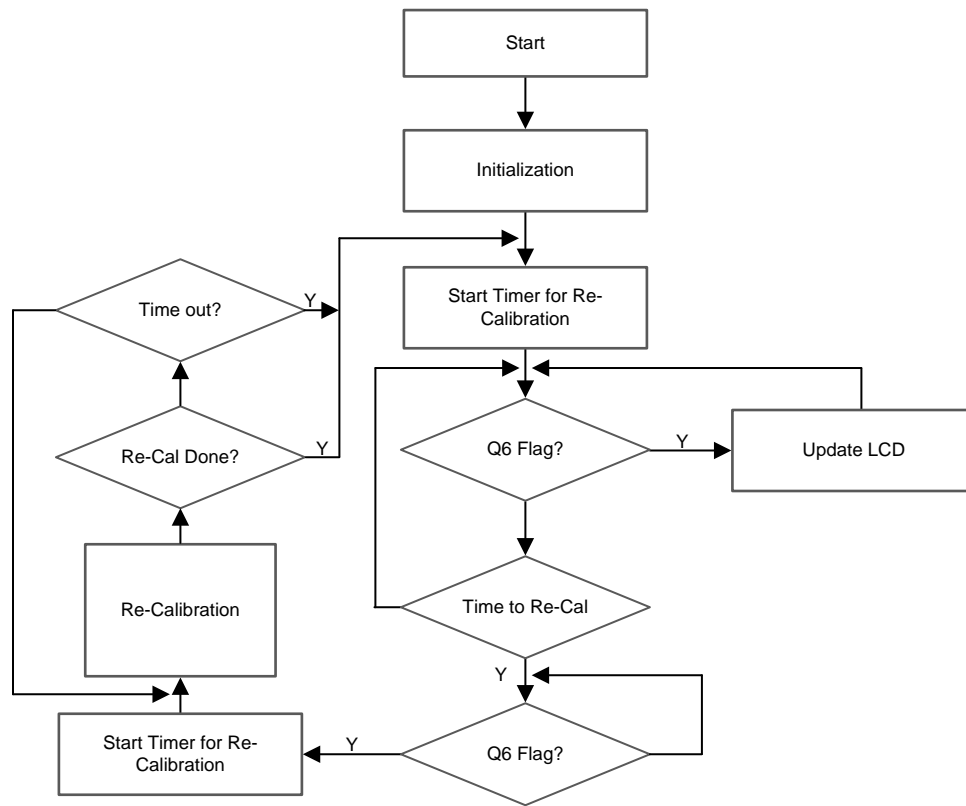


Figure 6. Software Flowchart

The software optimizes the system's power consumption. As shown in [Figure 6](#), the software starts with initialization, which includes port settings for low current leakage, LCD, ESI internal oscillator calibration, ESI registers, sampling rate, timing state machine (TSM) with auto-TSM calibration, optimal DAC level, and processing state machine (PSM) table setting. After initialization, the EVM can work well in low power mode with ESI and LCD as the only modules actively running. To avoid too many interrupts to wake up the CPU, the system uses the Q6 flag in the PSM table. This flag is set only when the rotor disc is rotating.

The system is in LPM3 mode when the rotor disc does not rotate. To lower the power consumption further, disable the LCD. Construct a key button to wake up the LCD when reading is necessary. For a stable, long-running lifetime for the system, the design includes a runtime re-calibration to track the drift of the sensors and system. A timer with the variable constant *Time_to_Recal* is used to count the period for re-calibration.

For a detail description, see [LC Sensor Rotation Detection with MSP430 Extended Scan Interface \(ESI\)](#).

6 Test Setup

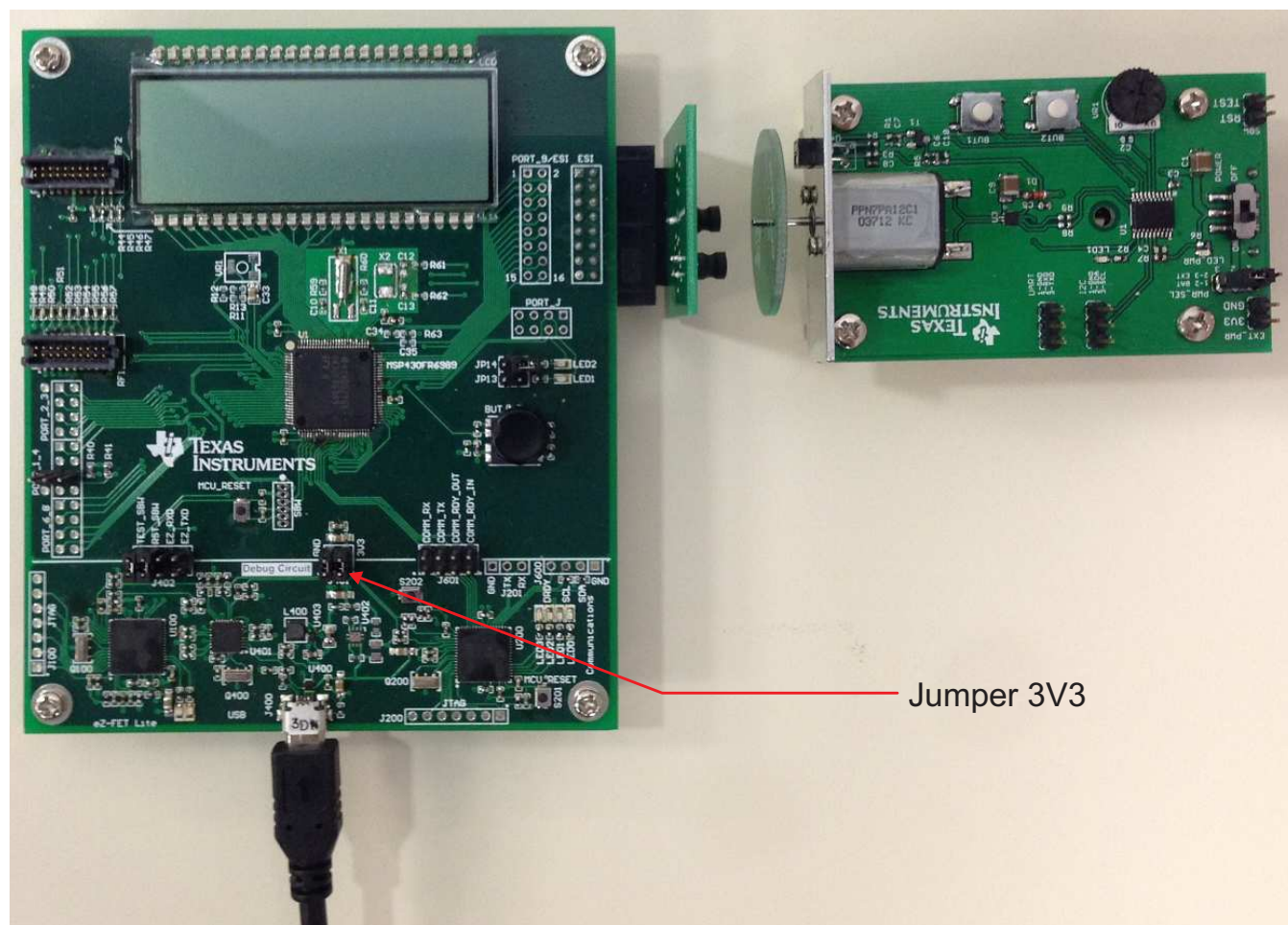


Figure 7. System Setup

Before testing, the main board and motor board have to be programmed with firmware. Follow this procedure to test the current consumption of the reference design:

1. Remove all jumpers of the main board except the jumper 3V3 and the ground jumper next to it.
2. Disconnect the jumper 3V3 and connect it with a current meter.
3. Set the rotor disc at 5 mm from the sensor board and switch off the motor.
4. Power up the main board with a USB cable.
5. Calibrate the TSM after powering up the main board. The LCD will show 0. wait until it turns to 8888, then go to the next step.
6. Switch on the motor and do not adjust the distance between the rotor and sensors. At this step, a calibration for searching proper reference voltages of DAC is working. This calibration will last for one second.
7. Finish initial calibration. The LCD will keep counting the number of rotations.
8. Turn off the LCD by pushing the black button.
9. Read the current meter indicating the current consumption of the reference design without the LCD.

7 Test Results

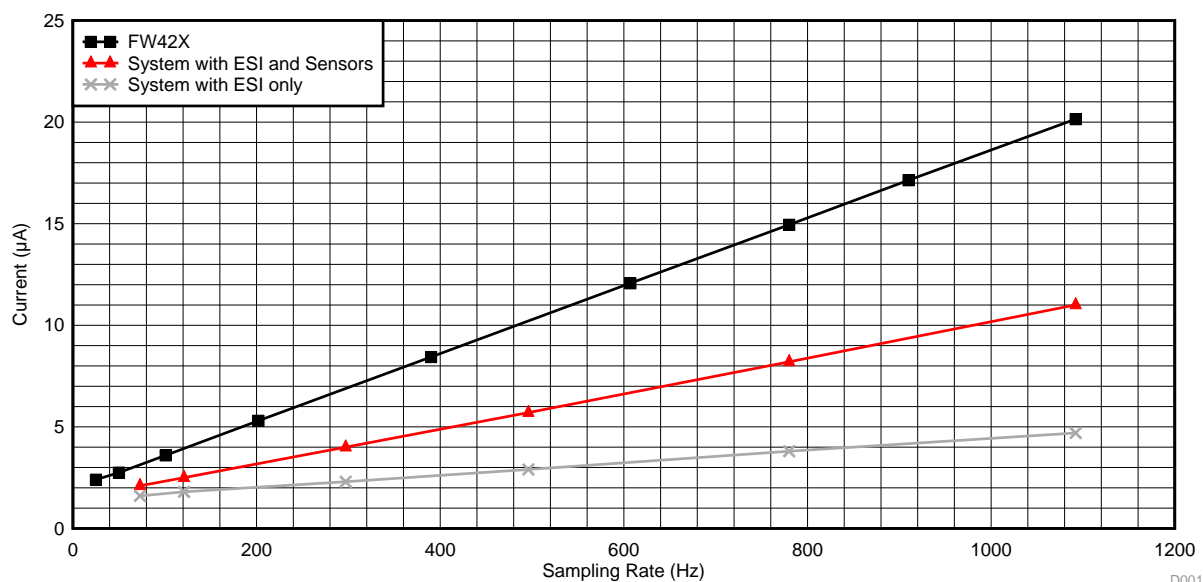


Figure 8. Test Results

Figure 8 shows the current consumption of the MCU with three LC sensors, not including all current flowing into the LCD, power, and other modules on the board. The data is taken by measuring the current flowing into the MCU connected to the two LC sensors with the LCD switched off, varying with different ESI sampling rates of the MSP430FR6989.

From the experimental data, the current consumption in the MSP430FR6989 takes 9 nA per sample with two LC sensors. Compared to the recorded data of 17 nA per sample from the MSP430FW42x system with the same type of LC sensors, the MSP430FR6989 has an improved power consumption.

The current consumption of the MSP430FR6989 running with ESI without sensors is also given. These results show that the LC sensors take half of the total current consumption of the system. To further reduce the current consumption, use well-designed LC sensors.

8 Design Files

8.1 Schematics

To download the schematics, see the design files at [TIDM-LC-WATERMTR](#).

8.1.1 Main Board without the Debugging Circuit


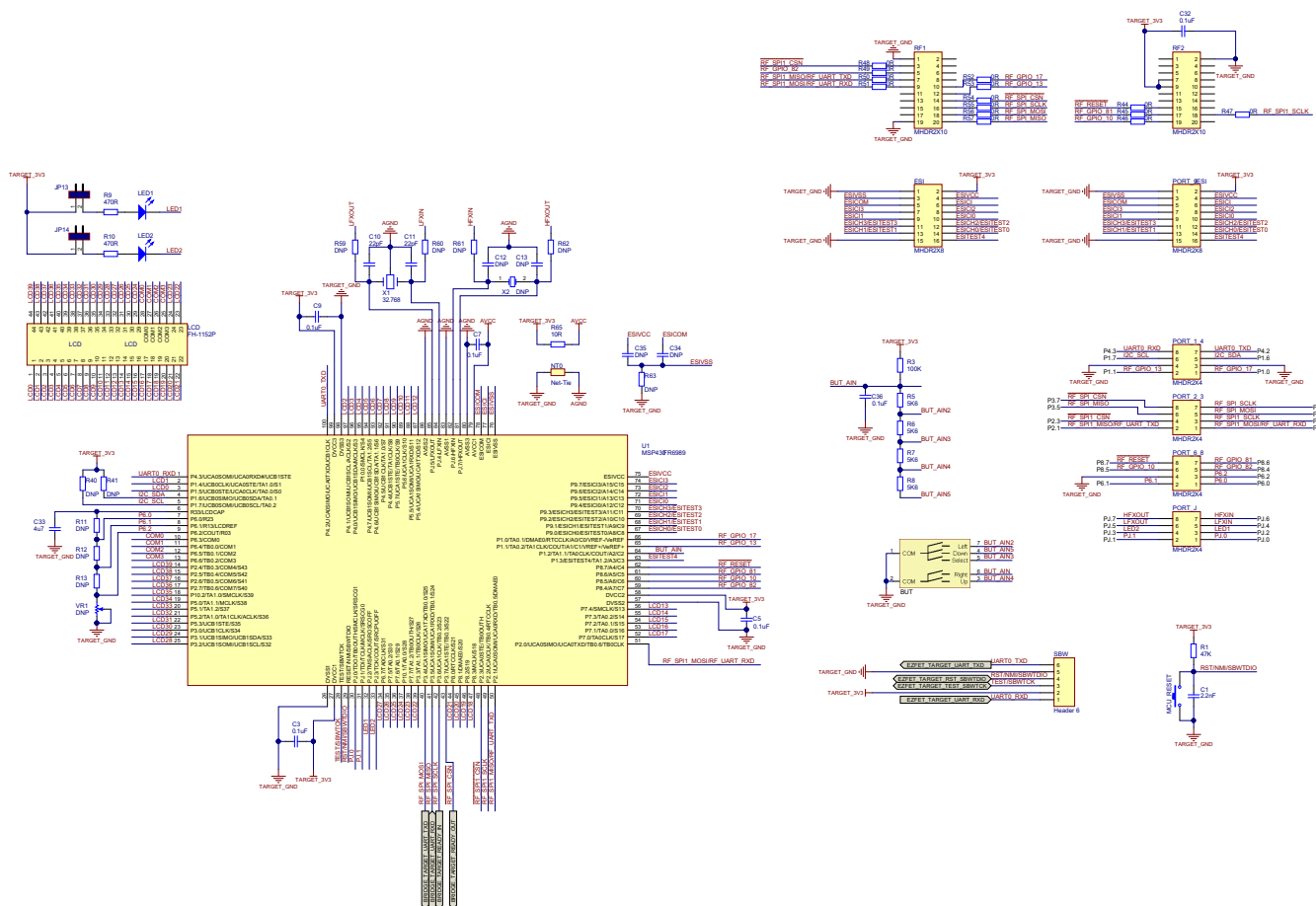


Figure 9. MSP430FR6989 Schematic

8.1.2 Sensor Board

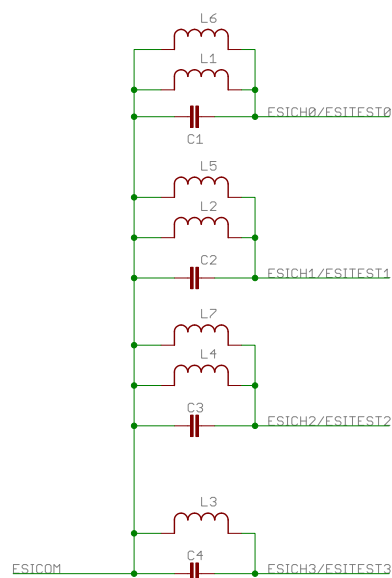

For 1 sensor
Place L1, C1
Use ESICH0

For 2 sensors
Place L1, L2, C1 and C2 (90 degree separation)
or L1, L5, C1 and C2 (45 degree separation)
Use ESICH0 and ESICH1

For 3 sensors
Place L2, L6, L7, C1, C2, C3
Use ESICH0, ESICH1 and ESICH2

For 4 sensors
Place L1, L2, L4, L3, C1, C2, C3, C4
Use ESICH0, ESICH1, ESICH2 and ESICH3

Inductor = 470uH
Capacitor = 220pF

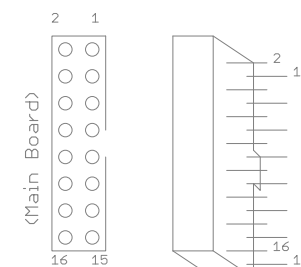
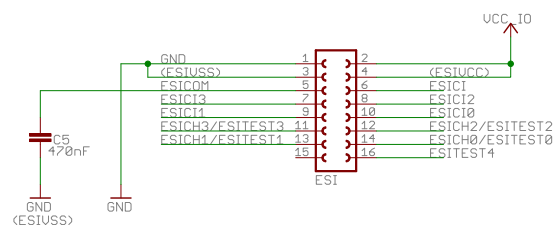


Figure 10. Sensor Board Schematic

8.1.3 Motor Board

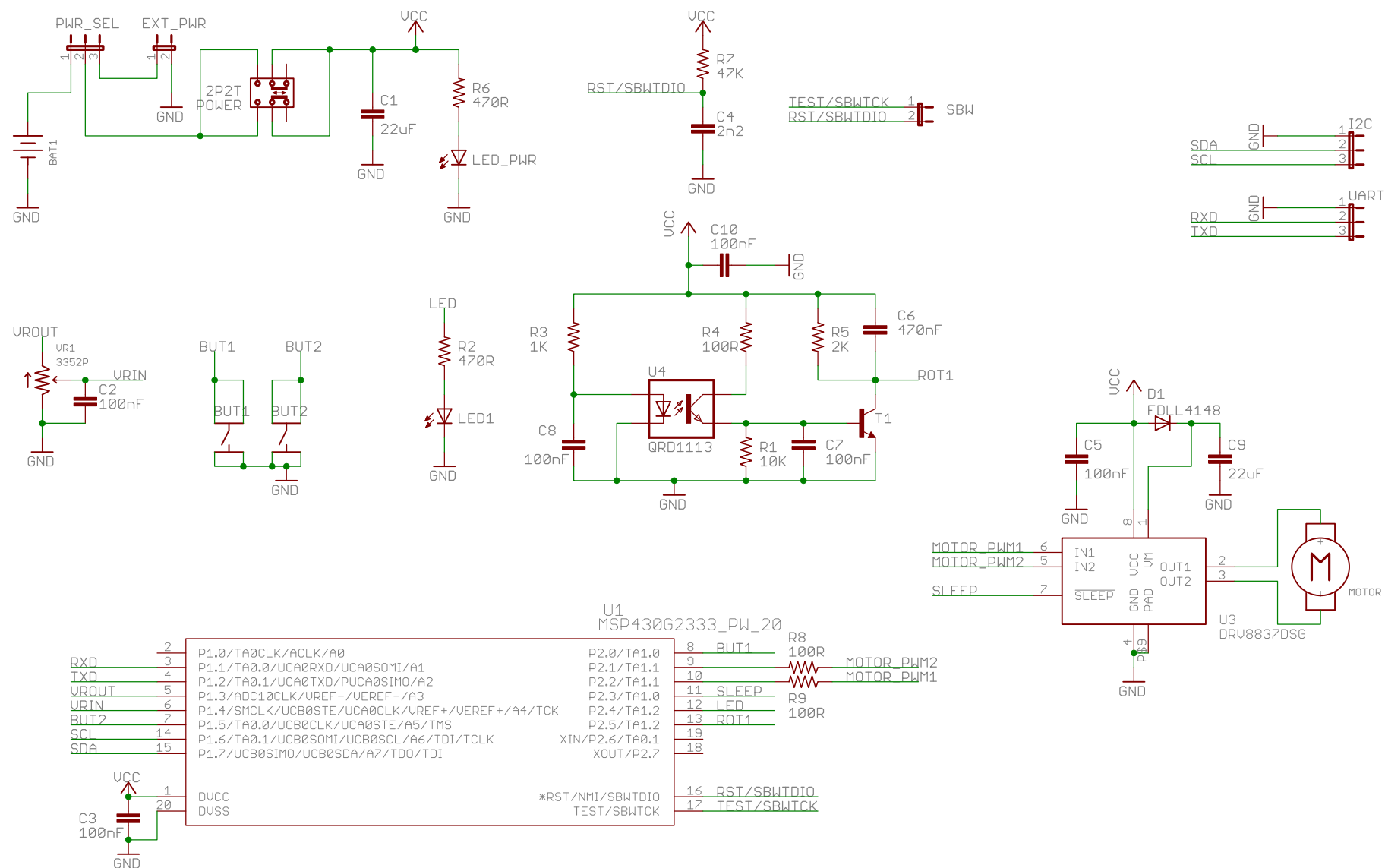


Figure 11. Motor Board Schematic

8.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDM-LC-WATERMTR](#).

Table 3. BOM: Main Board

DESIGNATOR	VALUE	QTY	DESCRIPTION	PACKAGE	MANUFACTURER PN	DIGIKEY PN	REMARK	MANUFACTURER
CAPACITORS								
C100, C101, C200, C201, C405, C406, C410, C412	10 pF (NP0/C0G)	8	Chip Capacitor, C0G, 50 V, $\pm 5\%$	C0402	GRM1555C1H100J A01D	490-5921-1-ND	Alternatives: NP0/C0G, 10 V, $\pm 5\%$ or better	Murata
C10, C11, C403, C404	22 pF (NP0/C0G)	4	Chip Capacitor, C0G, 50 V, $\pm 5\%$	C0402	GRM1555C1H220J A01D	490-5868-1-ND	Alternatives: NP0/C0G, 10 V, $\pm 5\%$ or better	Murata
C109, C110	33 pF (NP0/C0G)	2	Chip Capacitor, C0G, 50 V, $\pm 5\%$	C0402	GRM1555C1H330J A01D	490-5936-1-ND	Alternatives: NP0/C0G, 10 V, $\pm 5\%$ or better	Murata
C111, C210	1000 pF	2	Chip Capacitor, X7R, 50 V, $\pm 10\%$	C0402	GRM155R71H102 KA01D	490-1303-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
C1		1	Chip Capacitor, X7R, 100 V, $\pm 10\%$	C0402	GRM155R72A222 KA01D	490-6367-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
C3, C5, C7, C9, C32, C36, C102, C104, C108, C202, C204, C205, C400, C402, C407, C408	100 nF	16	Chip Capacitor, X7R, 16 V, $\pm 10\%$	C0402	GRM155R71C104 KA88D	490-3261-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
C105, C106, C206, C207	220 nF	4	Chip Capacitor, X7R, 16 V, $\pm 10\%$	C0402	GRM155R71C224 KA12D	490-5418-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
C107, C208	470 nF	2	Chip Capacitor, X5R, 10 V, $\pm 10\%$	C0402	GRM155R61A474 KE15D	490-3264-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
C411, C415, C417	1 μ F	2	Chip Capacitor, X7R, 25 V, $\pm 10\%$	C0603	GRM188R71E105 KA12D	490-5307-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
C33, C401	4.7 μ F	1	Chip Capacitor, X7R, 16 V, $\pm 10\%$	C0805	GRM21BR71C475 KA73L	490-4522-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
C103, C203, C209, C409	10 μ F	4	Chip Capacitor, X7R, 25 V, $\pm 10\%$	C1206	GRM31CR71E106 KA12L	490-6518-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
RESISTORS								

Table 3. BOM: Main Board (continued)

DESIGNATOR	VALUE	QTY	DESCRIPTION	PACKAGE	MANUFACTURER PN	DIGIKEY PN	REMARK	MANUFACTURER
R44, R45, R46, R47, R48, R49, R50, R51, R52, R53, R54, R55, R56, R57, R420	0 R	15	Chip Resistor	R0402	RC0402JR-070RL	311-0.0JRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R65	10 R	1	Chip Resistor	R0402	RC0402JR-0710RL	311-10JRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R407, R409, R412, R413, R416, R417	22 R	6	Chip Resistor	R0402	RC0402JR-0722RL	311-22JRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R100, R101, R201, R203, R406	27 R	5	Chip Resistor	R0402	RC0402JR-0727RL	311-27JRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R405	33 R	1	Chip Resistor	R0402	RC0402JR-0733RL	311-33JRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R211	100 R	1	Chip Resistor	R0402	RC0402JR-07100RL	311-100JRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R105, R202, R204, R205	390 R	4	Chip Resistor	R0402	RC0402JR-07390RL	311-390JRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R9, R10, R104, R200	470 R	2	Chip Resistor	R0402	RC0402JR-07470RL	311-470JRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R103, R206, R408	1.5 k	3	Chip Resistor	R0402	RC0402JR-071K5L	311-1.5KJRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R600, R601	2.2 k	2	Chip Resistor	R0402	RC0402JR-072K2L	311-2.2KJRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R40, R41	10 k	2	Chip Resistor	R0402	RC0402JR-0710KL	311-10KJRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R400, R401, R402, R403, R410, R411, R414, R415	15.0 k	8	Chip Resistor	R0402	RC0402JR-0715KL	311-15KJRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R1, R106, R209, R404	47 k	4	Chip Resistor	R0402	RC0402JR-0747KL	311-47KJRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R102, R210	1 M	2	Chip Resistor	R0402	RC0402JR-071ML	311-1.0MJRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R5, R6, R7, R8	5.6 k	4	Chip Resistor 1%	R0402	RC0402FR-075K6L	311-5.6KLRCT-ND	Alternatives: $\pm 1\%$ or better	Yageo
R3	100 k	1	Chip Resistor 1%	R0402	RC0402FR-07100KL	311-100KLRCT-ND	Alternatives: $\pm 1\%$ or better	Yageo
R109	150 k	1	Chip Resistor 1%	R0402	RC0402FR-07150KL	311-150KLRCT-ND	Alternatives: $\pm 1\%$ or better	Yageo
R107, R108	220 k	2	Chip Resistor 1%	R0402	RC0402FR-07220KL	311-220KLRCT-ND	Alternatives: $\pm 1\%$ or better	Yageo

Table 3. BOM: Main Board (continued)

DESIGNATOR	VALUE	QTY	DESCRIPTION	PACKAGE	MANUFACTURER PN	DIGIKEY PN	REMARK	MANUFACTURER
R110	240 k	1	Chip Resistor 1%	R0402	RC0402FR-07240KL	311-240KLRCT-ND	Alternatives: $\pm 1\%$ or better	Yageo
INDUCTORS, DIODES, CRYSTALS								
L400	2.2 μ H	1	SMD Inductor	3x3 mm	NR3010T2R2M	587-1638-1-ND		Taiyo Yuden
D100, D200	Red	2	LED, Red, SMD	603	LTST-C190CKT	160-1181-1-ND		Lite-On Inc
D101, D201, D202, D203	Green	4	LED, Green, SMD	603	LTST-C190GKT	160-1183-1-ND		Lite-On Inc
LED1, LED2	Amber	2	LED, Amber, SMD	603	LTST-C190AKT	160-1180-1-ND		Lite-On Inc
Q100, Q200	4 Mhz	2	Ceramic Resonator	CSTCR	CSTCR4M00G15L99-R0	490-7861-1-ND		Murata
Q400	6 Mhz	1	Ceramic Resonator	CSTCR	CSTCR6M00G55-R0	490-5997-1-ND		Murata
X1	32.768 kHz	1	Crystal Oscillator	Cylindrical Can, Radial	CMR200T-32.768KDZF-UT	300-8340-1-ND		Citizen
ICs								
U1	MSP430FR6989PZ	1	Mixed Signal Microcontroller	MSP430FR6989	MSP430FR6989	N/A	Provided by TI	Texas Instruments
U100, U200	MSP430F5528IRG C	2	Mixed Signal Microcontroller	TI_RGC0064B_N	MSP430F5528IRG CR	296-27930-1-ND		Texas Instruments
U400	TPD2E001DRL	1	15-kV ESD-Protection Array	DRL0005A	TPD2E001DRLR	296-21883-1-ND		Texas Instruments
U401	TUSB2046BIRHB	1	4-Port Full-Speed USB Hub	RHB0032E	TUSB2046BIRHBR	296-21926-1-ND		Texas Instruments
U403	TPS62237DRY	1	3.3-V Buck Step Down Regulator	DRY0006A	TPS62237DRYT	296-25630-1-ND		Texas Instruments
CONNECTORS								
J400	micro B	1	micro-USB Type B, Reverse, Receptacle, SMD, RA	CONN_USB_micro_ZX62R-B-5PA	ZX62R-B-5P	H11574CT-ND		Hirose
RF1, RF2	2x10 SMD	2	Header, SMD, 1.27 mm, 2x10	HDR2X10	TFM-110-02-SM-D-A-K	N/A	Contact Samtec directly	Samtec
(JP13+JP14), J401	2x2	2	Header, TH, 2.54 mm, 2x2	HDR2X2	67997-104HLF	609-3225-ND	Alternative: Any similar JP13 and JP14 share same component	FCI
J402, J601 PORT_1_4, PORT_2_3, PORT_6_8, PORT_J	2x4	6	Header, TH, 2.54 mm, 2x4	HDR2X4	67997-108HLF	609-3226-ND	Alternative: Any similar	FCI
ESI	2x8 RA	1	Shrouded Header, TH, 2.54 mm, 2x8, Right Angled	HDR2X8	SBH11-PBPC-D08-RA-BK	S9179-ND		Sullins Connector Solutions

Table 3. BOM: Main Board (continued)

DESIGNATOR	VALUE	QTY	DESCRIPTION	PACKAGE	MANUFACTURER PN	DIGIKEY PN	REMARK	MANUFACTURER
(Jumpers)	1x2	12	2-pin Jumper, 2.54 mm	N/A	QPC02SXGN-RC	S9337-ND	Alternative: Any similar	Sullins Connector Solutions
MISCELLANEOUS								
BUT	TPA511GLFS	1	4-Way Navigation Switch with select	TPA511GLFS	TPA511GLFS	401-1130-1-ND		C&K
BUT (Accessory)	Y43109100OP	1	Cap for TPA511GLFS	N/A	Y43109100OP	401-1997-ND		C&K
MCU_RESET, S201, S202	B3U-1000P	3	Push Button	B3U-1000P	B3U-1000P	SW1020CT-ND		Omron
LCD	FH-1152P	1	Custom 160-segment LCD	FH-1152P	FH-1152P	N/A	Provided by TI	ADKOM Elektronik GmbH
M3 Hex Standoff	M3/13 mm	4	M3 13 mm Female, female	N/A	Harwin Inc	952-1488-ND	Alternative: Any similar	R30-1011302
M3 Screw	M3/6 mm	4	M3 Screw Philips Pan Head Head Diameter 5 to 6 mm Thread Length 6 mm		RM3X8MM 2701	335-1149-ND	Alternative: Any similar M3 Screws	APM Hexseal

Table 4. BOM: Sensor Board (Two-LC Configuration)

DESIGNATOR	VALUE	QTY	DESCRIPTION	PACKAGE	MANUFACTURER PN	DIGIKEY PN	REMARK	MANUFACTURER
CAPACITORS								
C1 C2	220 pF (NP0/C0G)	2	Chip Capacitor, C0G, 50 V, ±5%	C0402	GRM1555C1H221 JA01D	490-1293-1-ND	Alternatives: NP0/C0G, 10 V, ±5% or better	Murata
C5	470 nF	1	Chip Capacitor, X5R, 10 V, ±10%	C0402	GRM155R61A474 KE15D	490-3264-1-ND	Alternatives: X5R, 10 V, ±10% or better	Murata
INDUCTORS								
L1 L2	470 µH	2		Radial	11R474C	811-2034-ND		Murata
CONNECTORS								
ESI	8x2	1	8x2 2.54-mm Female Socket		SFH11-PBPC-D08-ST-BK	S9196-ND		Sullins Connector Solution

Table 5. BOM: Motor Board

DESIGNATOR	VALUE	QTY	DESCRIPTION	PACKAGE	MANUFACTURER PN	DIGIKEY PN	REMARK	MANUFACTURER
RESISTORS								
R4, R8, R9	100 R	3	Chip Resistor	R0402	RC0402JR-07100RL	311-100JRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R2, R6	470 R	2	Chip Resistor	R0402	RC0402JR-07470RL	311-470JRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R3	1 K	1	Chip Resistor	R0402	RC0402JR-071KL	311-1.0KJRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R5	2 K	1	Chip Resistor	R0402	RC0402JR-072KL	311-2.0KJRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R1	10 K	1	Chip Resistor	R0402	RC0402JR-0710KL	311-10KJRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
R7	47 K	1	Chip Resistor	R0402	RC0402JR-0747KL	311-47KJRCT-ND	Alternatives: $\pm 5\%$ or better	Yageo
VR1	10 K	1	10-K POT		3352P-1-103LF	3352P-103LF-ND	Alternatives: Same type, value between 10 to 100 K	Bourns Inc.
CAPACITORS								
C4	2200 pF	1	Chip Capacitor, X7R, 100 V, $\pm 10\%$	C0402	GRM155R72A222 KA01D	490-6367-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
C3, C5, C7, C8, C10	100 nF	5	Chip Capacitor, X7R, 16 V, $\pm 10\%$	C0402	GRM155R71C104 KA88D	490-3261-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
C6	470 nF	1	Chip Capacitor, X5R, 10 V, $\pm 10\%$	C0402	GRM155R61A474 KE15D	490-3264-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
C1, C9	22 μ F	2	Chip Capacitor, X5R, 16 V, $\pm 20\%$	C1206	GRM31CR61C226 ME15L	490-4739-1-ND	Alternatives: X5R, 10 V, $\pm 10\%$ or better	Murata
DIODES, LEDs								
LED1	Red	1	LED, Red, SMD	603	LTST-C190CKT	160-1181-1-ND		Lite-On Inc
LED_PWR	Green	1	LED, Green, SMD	603	LTST-C190GKT	160-1183-1-ND		Lite-On Inc
D1	MBR0520L	1	0.5-A Schottky Diode, SMD	SOD123	MBR0520L	MBR0520LCT-ND		Fairchild
ICs, TRANSISTORS								
U1	MSP430G2553	1	MCU: MSP430G2553	20 TSSOP PW(R-PDSO-G20)	MSP430G2553IP W20	296-28430-1-ND		Texas Instruments
U3	DRV8837DSG	1	Low-Voltage H-Bridge Driver	DSG(S-PWSON-N8)	DRV8837DSGR	296-34786-1-ND		Texas Instruments

Table 5. BOM: Motor Board (continued)

DESIGNATOR	VALUE	QTY	DESCRIPTION	PACKAGE	MANUFACTURER PN	DIGIKEY PN	REMARK	MANUFACTURER
U4	QRD1113	1	Reflective Optical Sensor	Custom 4L	QRD1113	QRD1113-ND		Fairchild
T1	BC817-40L	1	NPN Transistor	SOT23	BC817-40L	BC817-40LT3GOSCT-ND		On Semi
JUMPERS, CONNECTORS, SWITCHES								
BUT1, BUT2		2	SMD push button	6x6 mm	B3SL-1002P	SW1064CT-ND		Omron
POWER	2P2T	1	SMD 2P2T Switch		JS202011SCQN	401-2002-1-ND		C&K Components
PWR_SEL, I2C, UART	3x1	3	3x1 2.54-mm Pin header		68001-103HLF	609-3468-ND		FCI
EXT_PWR, SBW	2x1	2	2x1 2.54-mm Pin header		68001-102HLF	609-3506-ND		FCI
(Jumpers)	1x2	1	2-pin Jumper, 2.54 mm	N/A	QPC02SXGN-RC	S9337-ND		Sullins Connector Solutions
MISCELLANEOUS								
Motor		1	Motor		PPN7PA12C1	P14355-ND		NMB Technologies Corporation
BAT	2xAAA	1	2xAAA Battery holder		2468	2468K-ND		Keystone Electronics
Motor Mount		1	Custom made motor mount		N/A	N/A		N/A
M2 Screws	M2/3 mm	2	M2 Screw Philips Pan Head Head Diameter 3 mm Head Height 1 mm Thread Length 3 mm Total length 4 mm			N/A		
M2 Spring	M2/4-mm dia	2	M2 Spring Diameter around 4 mm Thickness <1 mm		MLWZ 002	H771-ND		B&F Fastener Supply
M3 Screw	M3/6 mm	5	M3 Screw Philips Pan Head Head Diameter 5 to 6 mm Thread Length 6 mm		RM3X8MM 2701	335-1149-ND		APM Hexseal
M3 Hex Standoff	M3/2.54 cm	4	M3 1-inch Standoff Female, female		R6397-02	952-2177-ND		Harwin Inc
M3 Nuts	M3	1	M3 Nut Width around 5 mm Thickness around 2 mm (for Mounting Battery Holder)			N/A		

8.3 PCB Layouts

To download the layer plots, see the design files at [TIDM-LC-WATERMTR](#).

8.3.1 Main Board

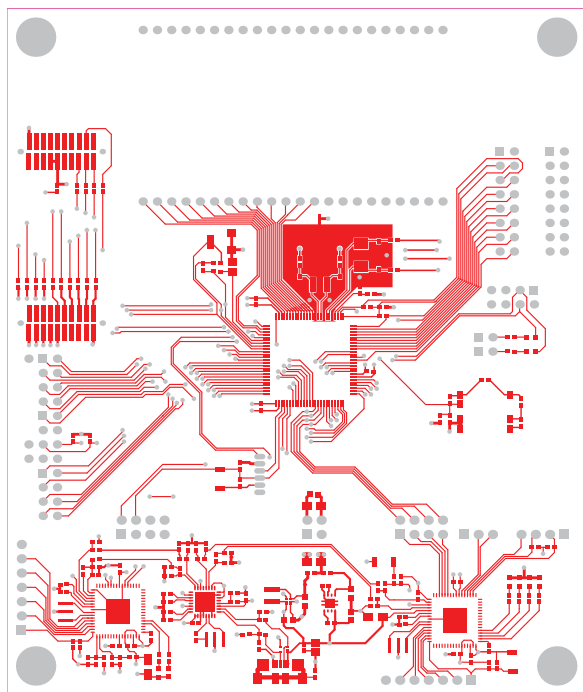


Figure 12. Main Board 1

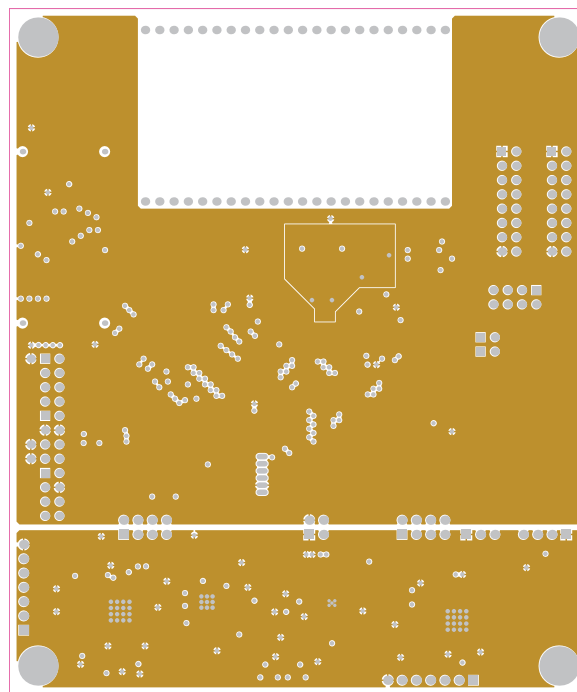


Figure 13. Main Board 2

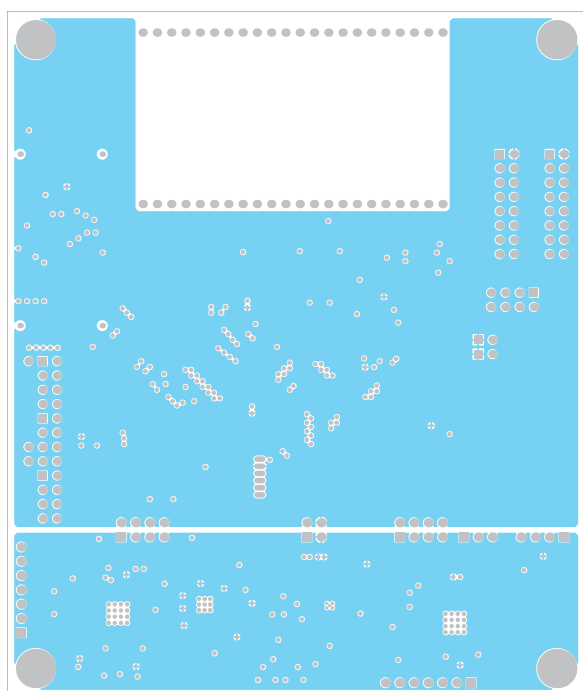


Figure 14. Main Board 3

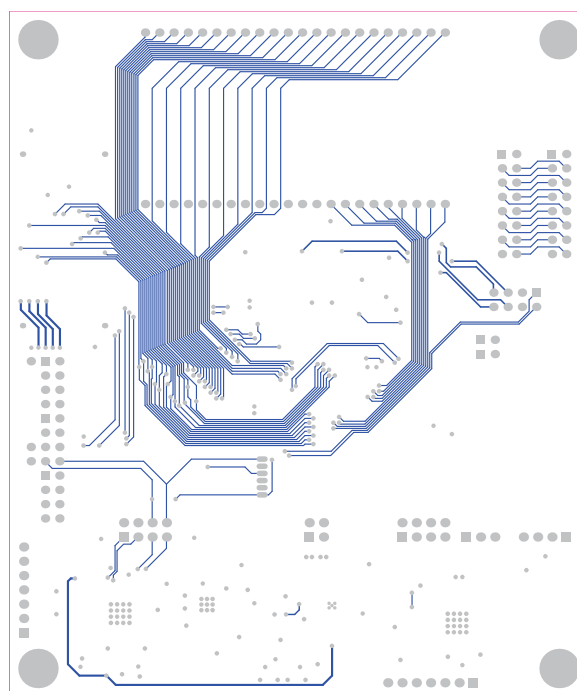


Figure 15. Main Board 4



8.3.2 Sensor Board

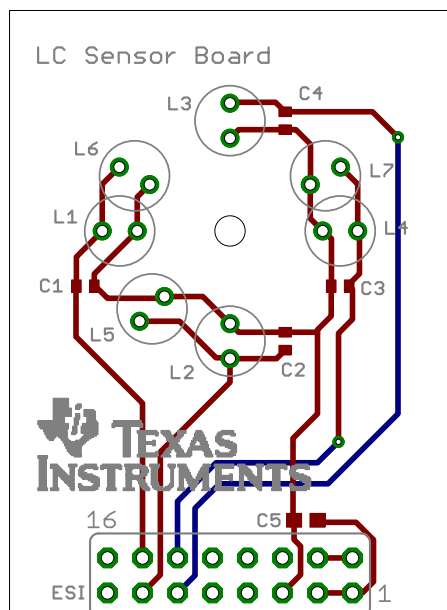


Figure 18. All Layers

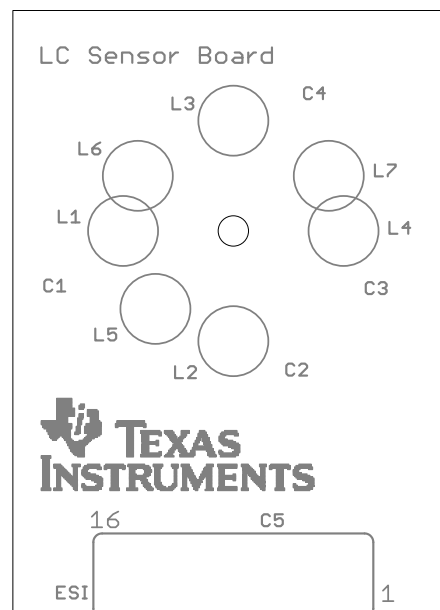


Figure 19. Top Silkscreen

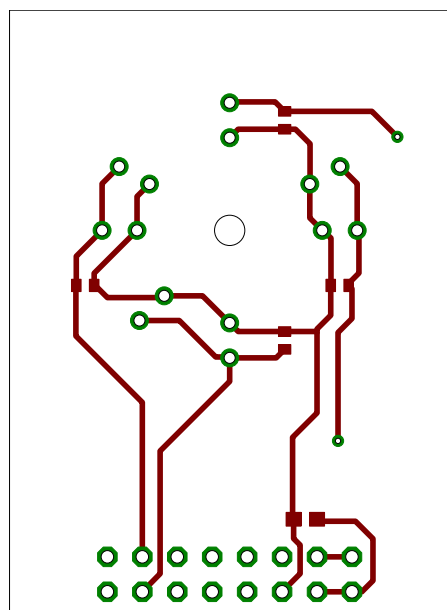


Figure 20. Component Side

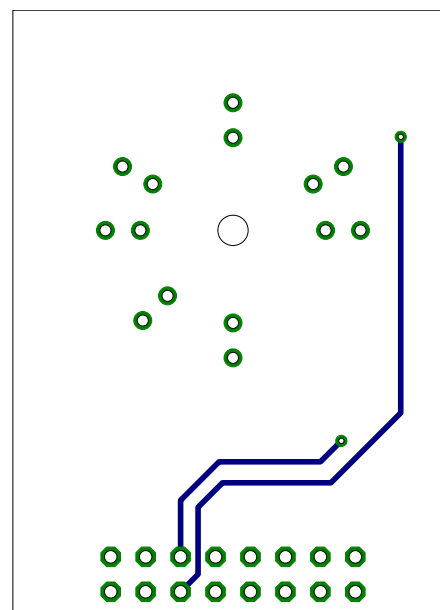


Figure 21. Solder Side

8.3.3 Motor Board

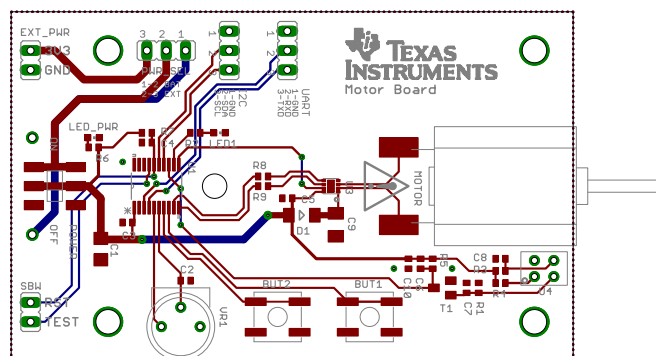


Figure 22. Motor Board 1

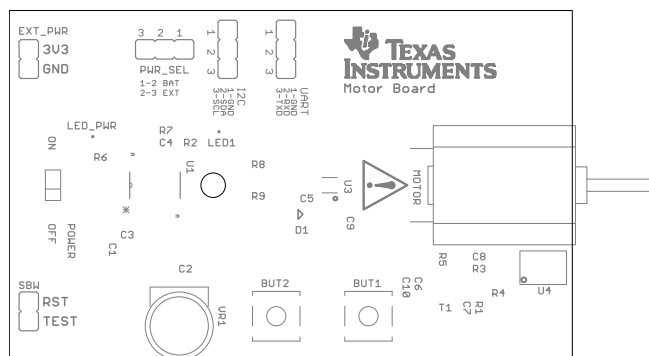


Figure 23. Motor Board 2

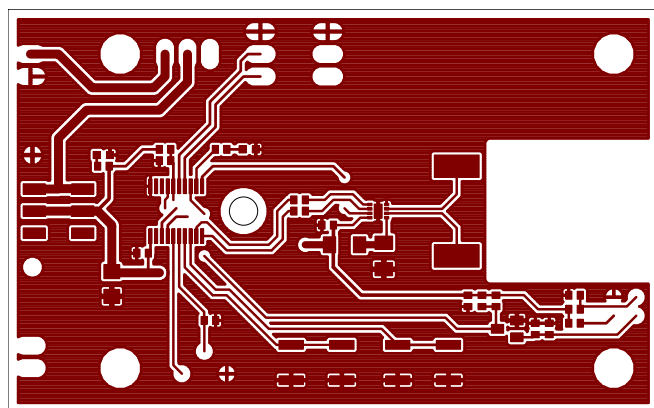


Figure 24. Motor Board 3

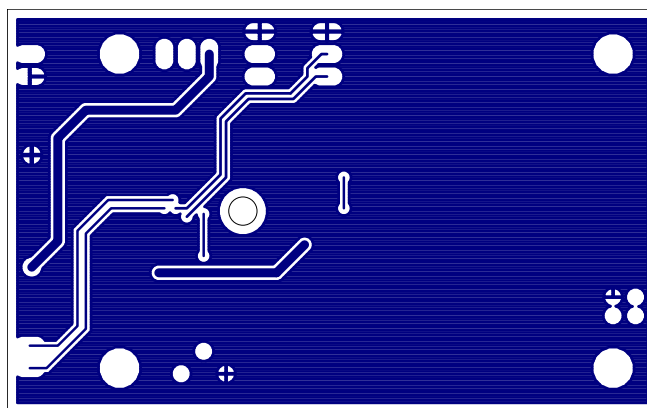


Figure 25. Motor Board 4

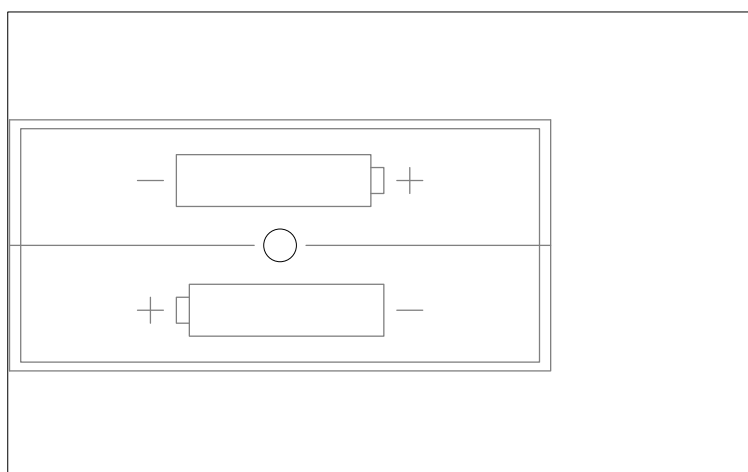


Figure 26. Motor Board 5

8.4 Altium Project

To download the Altium project files, see the design files at [TIDM-LC-WATERMTR](#).

8.5 Gerber Files

To download the Gerber files, see the design files at [TIDM-LC-WATERMTR](#).

8.6 Software Files

To download the software files, see the design files at [TIDM-LC-WATERMTR](#).

9 About the Author

THOMAS KOT is a system and solutions architect in the Smart Grid and Energy group at Texas Instruments, where he primarily works on the flow meter reference design development and customer support. Thomas received his bachelor of engineering in electronic engineering and his master of science in electronic and information engineering from Hong Kong Polytechnic University in 1995 and 2005, respectively. He received the master of business administration from City University of Hong Kong in 2007.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.